

Lab 3 CE100

Calculate sum or difference of two numbers represented in 8-bit 2's comp

$$a[7:0] = sw[7] \text{ to } sw[0]$$


$$b[7:0] = sw[15] \text{ to } sw[8]$$

$$b[n] = s[0]$$

$$sub = b[n] \cup$$


$$\text{overflow} = \text{clp}$$

m4 - 1 e in: in[3:0], sel[1:0], e
out: o

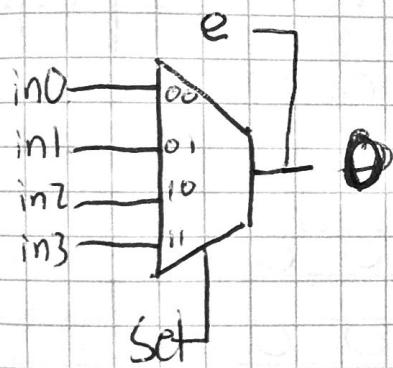

sel1	sel0	in3	in2	in1	in0	e	o	
0	0	0	0	0	1	0	0	
0	1	0	0	1	0	0	0	
1	0	0	1	0	0	0	0	
0	0	0	0	0	0	1	in0	
0	0	0	0	0	1	0	1	in1
1	0	0	0	1	0	1	1	in2
1	0	0	0	0	0	0	1	in3

m8 - 1 e in: in[7:0], sel[2:0], e
out: o

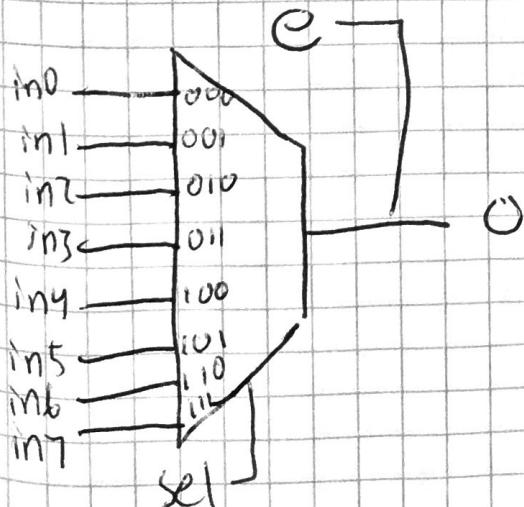

~~Lab 3~~
~~7/10~~

Truth Table
on next pg


✓ ✓ ✓
✓ ✓ ✓
✓ ✓ ✓
✓ ✓ ✓

M8-1e truth table

CE100 Lab 3

M2 - 1x8



in: in0[7:0], in1[7:0], sel
out: o[7:0]

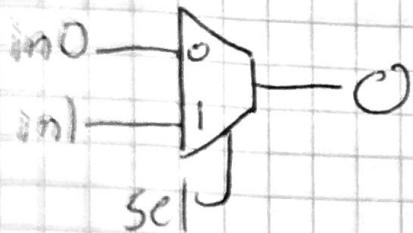

sign extend sel to
be 8 bits

AddSub8 in: A[7:0], B[7:0], sub
out: S[7:0], out1

sel ²	sel0	sum
00	00	00
01	10	00
10	00	00
11	00	00
00	00	00
01	01	00
10	01	00
11	11	00

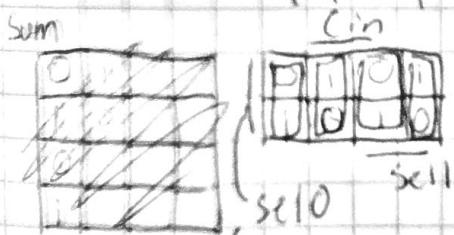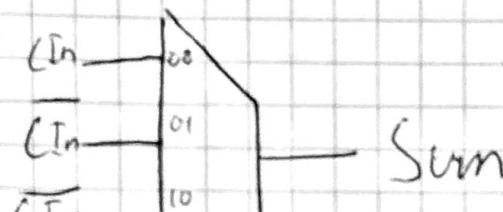

Full
Adder

in: sel0, sel1,
Cin
out: Cout, sum
enable tied
hi


8 bit Adder implemented next page

Overflow logic

S[7]	A[7]	B[7]
1	0	0
0	1	1


CE100 Lab 3

Add/Sub 8 8-bit adder $B = B_{sel}$

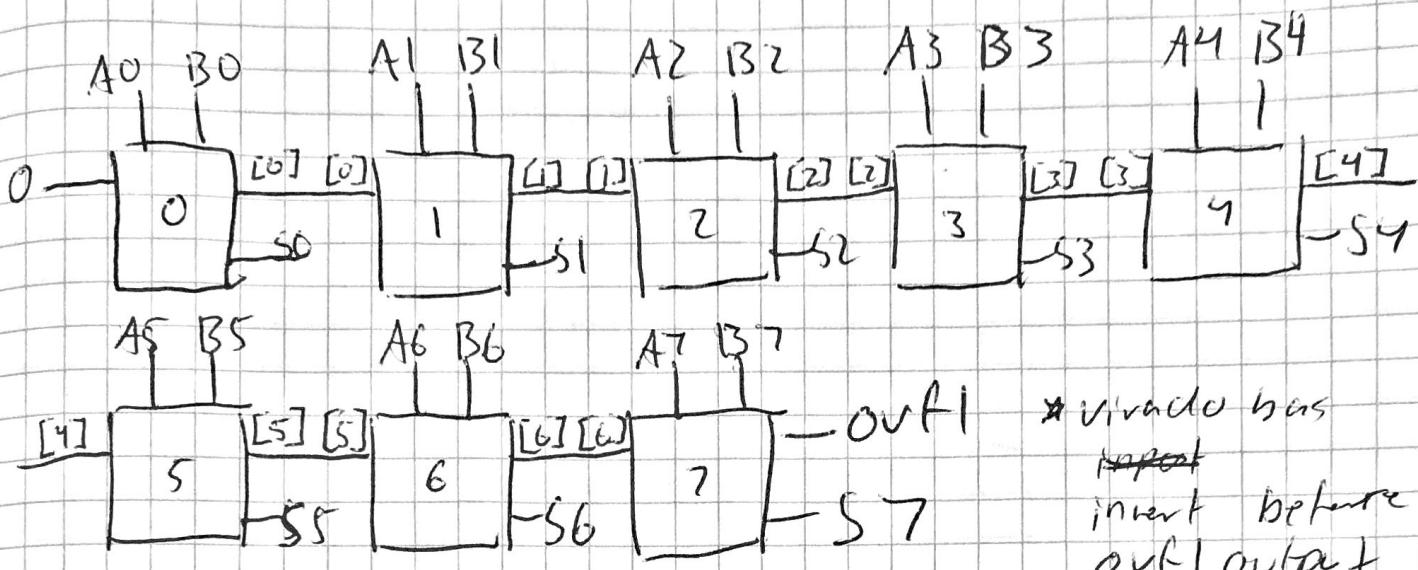

* mirando las
* invert before
* invert before
out1 output

Add/Sub 8 m2-1x80

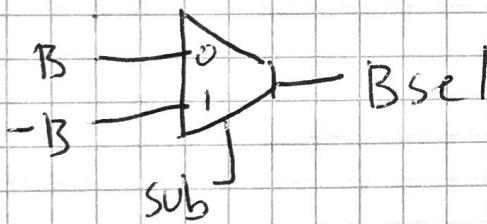


m2 hex⁷ seg in: n[3:0], c
out: seg[6:0]

Continued Next Pg

CE100 Lab 3

hex7seg m8_1e


#	n_3	n_2	n_1	n_0	A	B	C	D	E	F	G	6
0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1	0
3	0	0	1	1	1	1	1	1	0	0	1	1
4	0	1	0	0	0	1	1	0	0	1	1	1
5	0	1	0	1	1	0	1	1	0	1	1	1
6	0	1	1	0	1	0	1	1	1	1	1	1
7	0	1	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1	1
10	A	1	0	1	0	1	1	1	0	0	1	1
11	B	1	0	1	1	1	1	1	0	1	1	1
12	C	1	1	0	0	0	1	1	1	1	1	1
13	D	1	1	0	1	0	1	1	1	1	1	0
14	E	1	1	1	0	1	0	0	1	1	1	1
15	F	1	1	1	1	1	0	0	0	1	1	1

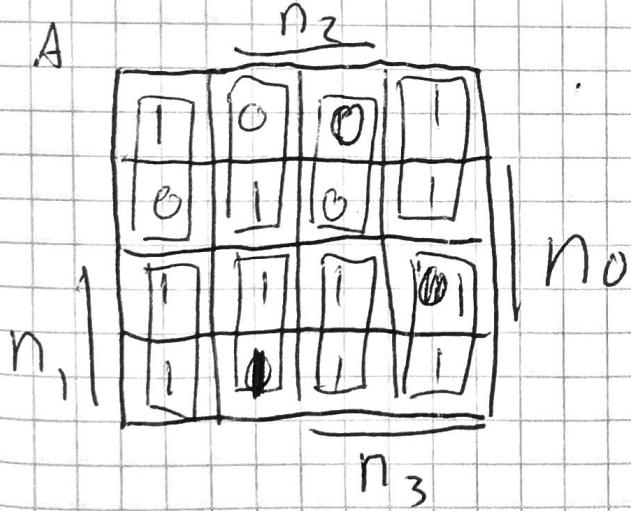

PEs

$\sim n[0], 1, n[0], 1, 1, \sim n[0], 1$,
 $\sim n[0], 1, 0$

0

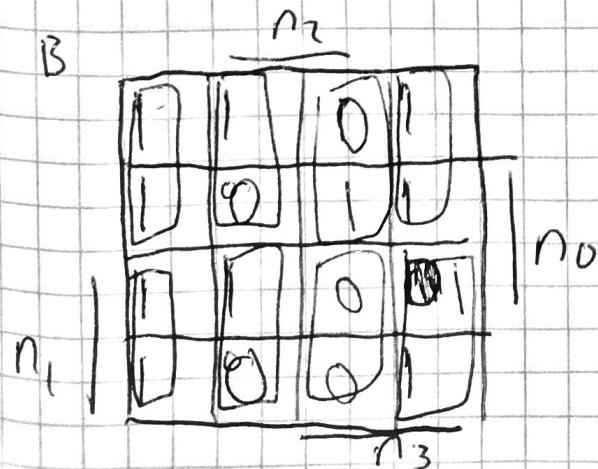


PEs

1, 1, $\sim n[0], n[0], 1, 1, n[0], 1$,
0

CE100 Lab 3


c $\overline{n_2}$

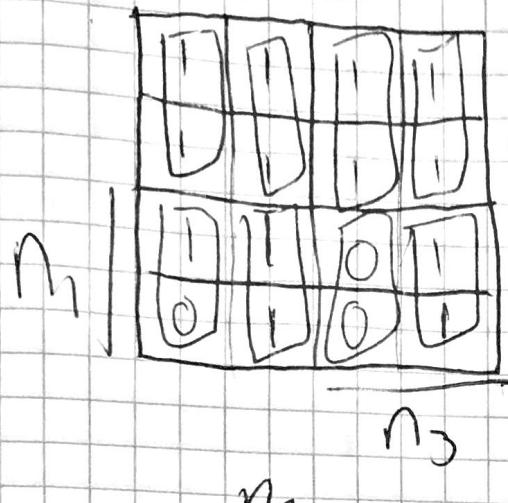

PIs

| no | 1, n[0], 1, 1, 1, 1, 1, 0


d $\overline{n_2}$

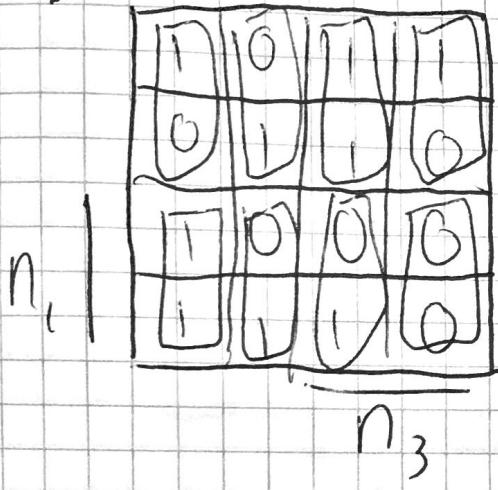

PIs

| no | ~n[0], 1, n[0], ~n[0], ~n[0], 0, 1, ~n[0]


e $\overline{n_2}$

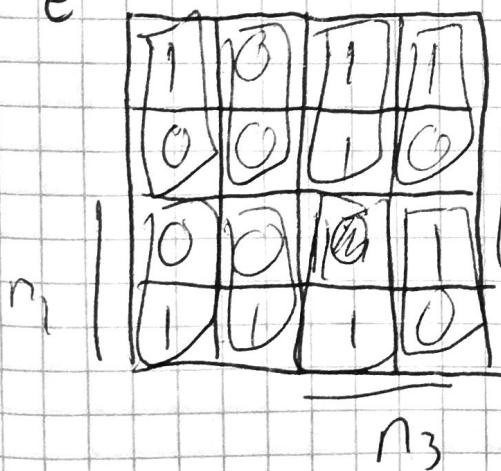

PIs


| no | ~n[0], ~n[0], 0, ~n[0], & ~n[0], ~n[0], n[0], 1, 1

CE100 Lab 3

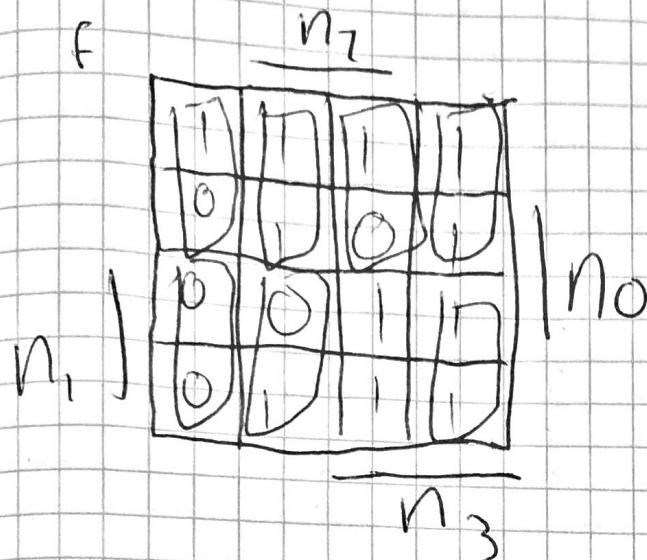

PIs

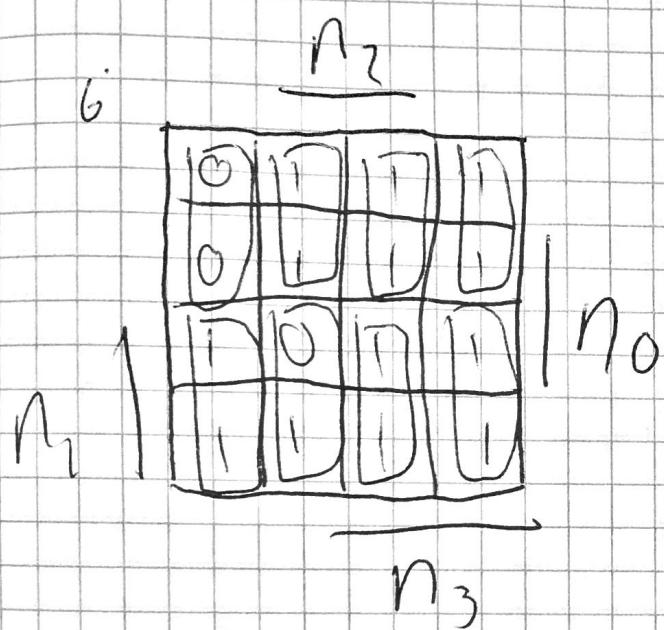$\sim n[0], 0, 1, \sim n[0], 1, 1$
 $\sim n[0], 1$




PIs

$0, 1, 1, \sim n[0], 1, 1, 1, 1$

~~Top level schematic~~

Lab 3 Top in: [15:0] sw, bInV, bInR, CLK, n_{in}
 out: seg[6:0], dP, Qn[3:0]

Add/Sub 80

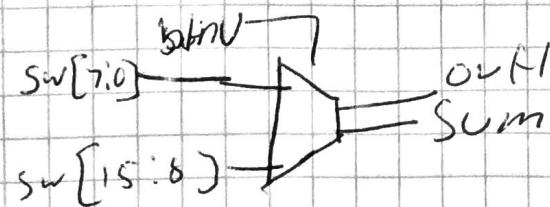

Lab 3 CE100

hex7seg011

in n₃ n₂ n₁ n₀

sum₃ 2 1 0 / 17654


in c

dig-set / dig-set

out seg

seg0 / seg1

m2 - 1x81

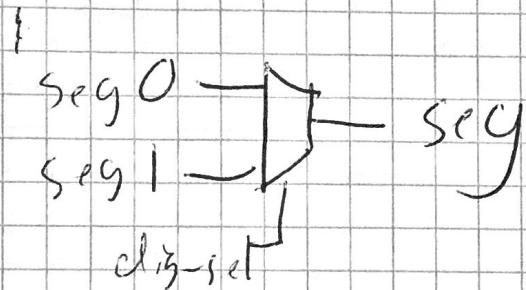

Lab 3 Sim

CE100 Lab 3

Top Level Design

