
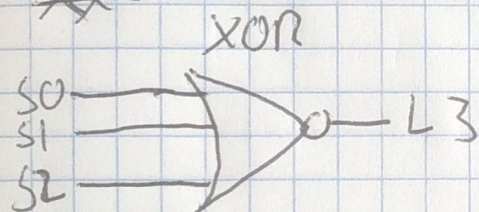
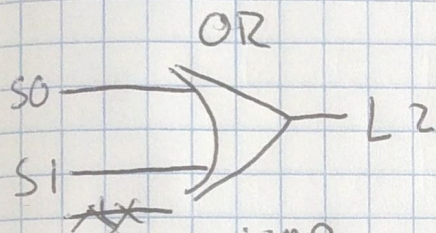
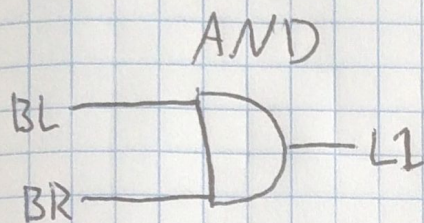


CE100 Lab 1

Justin Fortner
10/31/17 1:30


Part 2

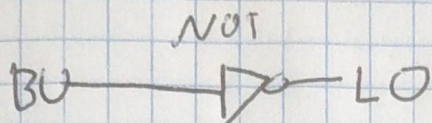Part 2: 25/08 TU-Th 1:30
✓✓
Good work
2:30pm



The elaborated design showed that Vivado only likes to display gates with no more than two inputs.

Vivado

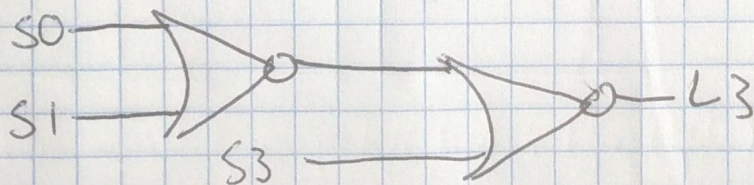

my design